

Lab Manual**Experiment No. 2****Combinational Circuits: Structural Modelling using Vivado**


DSD Lab Manual Evaluation Rubrics
--

Assessment	Total Marks	Marks Obtained	0-30%	30-60%	70-100%
Code Organization (CLO1)	3		No Proper Indentation and descriptive naming, no code organization. Zero to Some understanding but not working	Proper Indentation or descriptive naming or code organization. Mild to Complete understanding but not working	Proper Indentation and descriptive naming, code organization. Complete understanding, and proper working
Simulation (CLO2)	5		Simulation not done or incorrect, without any understanding of waveforms	Working simulation with errors, don't cares's(x) and high impedance(z), partial understanding of waveforms	Working simulation without any errors, etc and complete understanding of waveforms


FPGA (CLO2)	2		Not implemented on FPGA and questions related to synthesis and implementation not answered.	Correctly Implemented on FPGA or questions related to synthesis and implementation answered.	Correctly Implemented on FPGA and questions related to synthesis and implementation answered.
-------------	---	--	---	--	---

Experiment # 02

Schematic Diagram:

 

Implemented Circuit:

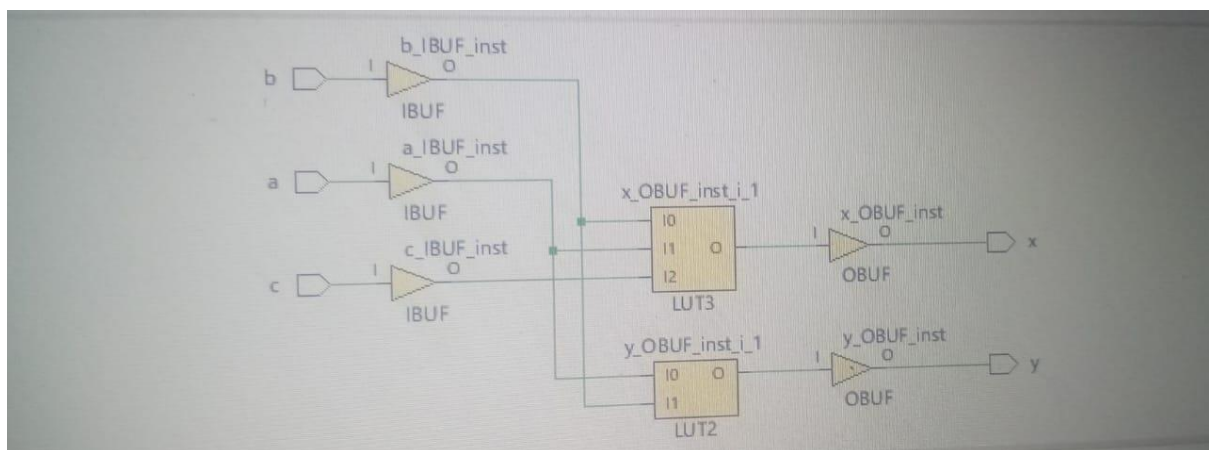

TASK 1(A)

Truth Table of the above circuit is shown as follows:

a	b	c	c'	a + b	(a.b)'	$z = (a.b)' \oplus (a + b)$	$x = c' \oplus (a + b)$	$y = z . (a + b)$
0	0	0	1	0	1	1	1	0
0	0	1	0	0	1	1	0	0
0	1	0	1	1	1	0	0	0
0	1	1	0	1	1	0	1	0
1	0	0	1	1	1	0	0	0
1	0	1	0	1	1	0	1	0
1	1	0	1	1	0	1	0	1
1	1	1	0	1	0	1	1	1

(A) Truth table for output x and y

TASK 1(B)

Max combinational delay = 3.66

Min combinational delay = 2.855

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	3	2	1	c	x	9.018	5.358	3.660	∞	input port clock
Path 2	∞	3	2	2	b	y	7.994	5.139	2.855	∞	input port clock

TASK 1(C)

```

143 7. Primitives
144 -----
145
146 +-----+-----+-----+
147 | Ref Name | Used | Functional Category |
148 +-----+-----+-----+
149 | IBUF      | 3    | IO                  |
150 | OBUF      | 2    | IO                  |
151 | LUT3      | 1    | LUT                 |
152 | LUT2      | 1    | LUT                 |
153 +-----+-----+-----+
154
155

```

SYSTEM VERILOG CODE

```
1
2  module design_file(
3      input a,
4      input b,
5      input c,
6      output x,
7      output y
8  );
9      assign or_out = a | b;
10     assign x = (~c) ^ or_out;
11     assign xor_out = ~(a & b) ^ (or_out);
12     assign y = or_out & xor_out;
13 endmodule
```